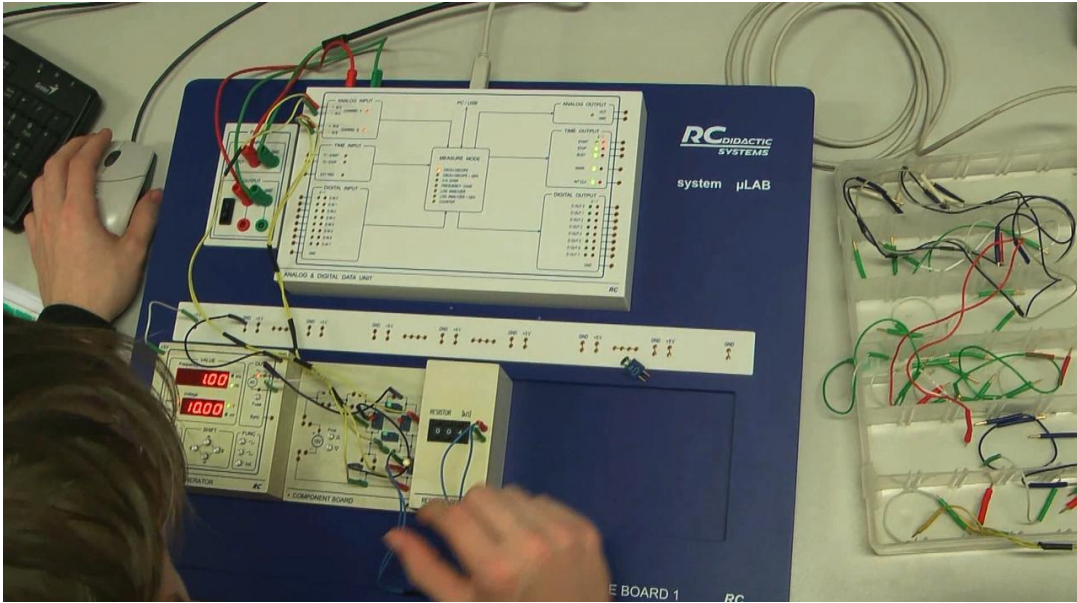


RC Didactic – Dvoucestný usměrňovač



Graetzův můstek s LED

Jméno

RC


Legend	Edit	Delete
A	Vstupní napětí	
B1	Bez filtru R = 5k	
B2	C = 10u a R = 44k	
B3	C = 10u a R = 88k	
B4	C = 10u a R = 100k	

Function	Trigger
Trigger	Source
Cursor	Slope
Measure	Level
Math	Ext
Utility	Off

Status	File
Stop	Open
Trig A	Save
0.0V	Print
	Exit

View			
YT	XY	Phasor	Harmonic

Init

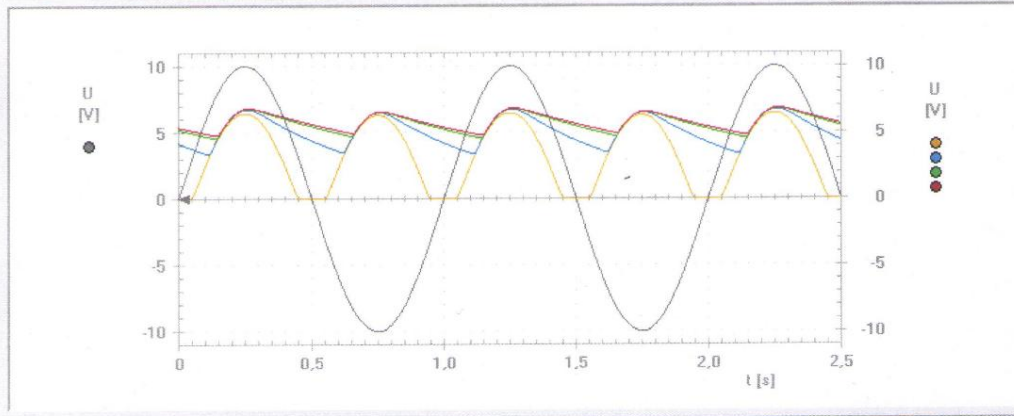

Measurement	Time	Gain	Average
Normal	Fun: Single	Sequence	Off
		B1 B2 B3 B4 Clr	
		A	
		B	